

BEE Experiments Record

10. VERIFICATION & INTERPRETATION OF LOGIC GATES.

★ PRE - LAB QUESTIONS \implies

① Name the different Logic Gates.

\rightarrow A Logic Gate is an idealized model of computation or physical electronic device implementing a Boolean function, a logical operation performed on one or more binary inputs that produces a single binary output.

The different Logic Gates are as follows:

- 1> AND
- 2> OR
- 3> NOT
- 4> NAND
- 5> NOR
- 6> X-OR (Exclusive OR)
- 7> X-NOR (Exclusive NOR)

② List out the IC names for different Logic Gates.

\rightarrow The IC names for different Logic Gates are as follows:

- 1> AND Gate \longrightarrow IC = 7408
- 2> OR Gate \longrightarrow IC = 7432
- 3> NOT Gate \longrightarrow IC = 7404
- 4> NAND Gate \longrightarrow IC = 7400
- 5> NOR Gate \longrightarrow IC = 7402
- 6> X-OR Gate \longrightarrow IC = 7486
- 7> X-NOR Gate \longrightarrow IC = 74266

③ What is the Boolean expression for a NOR Gate?

\rightarrow The Boolean expression for NOR Gate is as follows:

$$Y = \overline{A+B}$$

④ How does a NOR Gate work?

→ The NOR Gate is a digital logic gate that implements logical NOR - it behaves according to the truth table. A HIGH output (1) results if both the inputs to the gate are Low (0); if one or both input is HIGH (1), a Low output (0) results.

NOR is the result of the negation of OR operator.

It follows: $y = \overline{A+B}$ as Boolean equation.

Its Truth-Table is as follows:

INPUT		OUTPUT
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

⑤ Expression for EX-OR and EX-NOR?

→ 1) The Boolean expression for EX-OR: $y = A \oplus B$

$$\text{so, } y = A \oplus B = \overline{A} \cdot B + A \cdot \overline{B}$$

2) The Boolean expression for EX-NOR: $y = \overline{A \oplus B}$

$$\text{so, } y = \overline{A \oplus B} = \overline{\overline{A} \cdot B + A \cdot \overline{B}}$$

★ AIM \Rightarrow

To verify the Boolean expression using Logic Gates.

★ APPARATUS REQUIRED \Rightarrow


Logic trainer kit, Logic Gates / ICs, wires.

★ POST - LAB QUESTIONS \implies

① Name the Universal Gates?

 \rightarrow The Universal Gates are NAND and NOR.

② What is the symbol of NAND Gate?

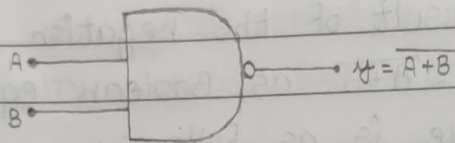 \rightarrow The symbol of NAND Gate is as follows:

③ How many NAND Gates are required to make an OR Gate?

 \rightarrow Three NAND Gates are required to make an OR Gate.

④ How many NOR Gates are required to implement a NAND Gate?

 \rightarrow Four NOR Gates are required to implement a NAND Gate.